

CEG3155: DGD 3

Questions

Question 1


- Convert the structural VHDL code shown below into schematic.
- Fill the truth table for the schematic from part a).

```


1  -- 2-to-4 Line Decoder; structural VHDL Description
2  library ieee;
3  use ieee.std_logic_1164.all
4
5  entity decoder_2_4_w_enable is
6  port(
7      EN, A0, A1 : in std_logic;
8      D0, D1, D2, D3 : out std_logic
9  );
10 end decoder_2_to_4_w_enable;
11
12 architecture structural1_1 of decoder_2_to_4_w_enable is
13     component NOT1
14     port(
15         in1: in std_logic;
16         out1: out std_logic
17     );
18     end component;
19
20     component AND2
21     port(
22         in1, in2: in std_logic;
23         out1: out std_logic
24     );
25     end component;
26
27     signal A0_n, A1_n, N0, N1, N2, N3: std_logic;
28     begin
29         g0: NOT1 port map (in1 => A0, out1 => A0_n);
30         g1: NOT1 port map (in1 => A1, out1 => A1_n);
31         g2: AND2 port map (in1 => A0_n, in2 => A1_n, out1 => N0);
32         g3: AND2 port map (in1 => A0, in2 => A1_n, out1 => N1);
33         g4: AND2 port map (in1 => A0_n, in2 => A1, out1 => N2);
34         g5: AND2 port map (in1 => A0, in2 => A1, out1 => N3);
35         g6: AND2 port map (in1 => EN, in2 => N0, out1 => D0);
36         g7: AND2 port map (in1 => EN, in2 => N1, out1 => D1);
37         g8: AND2 port map (in1 => EN, in2 => N2, out1 => D2);
38         g9: AND2 port map (in1 => EN, in2 => N3, out1 => D3);
39     end structural_1;
40

```

EN	A1	A0	D0	D1	D2	D3

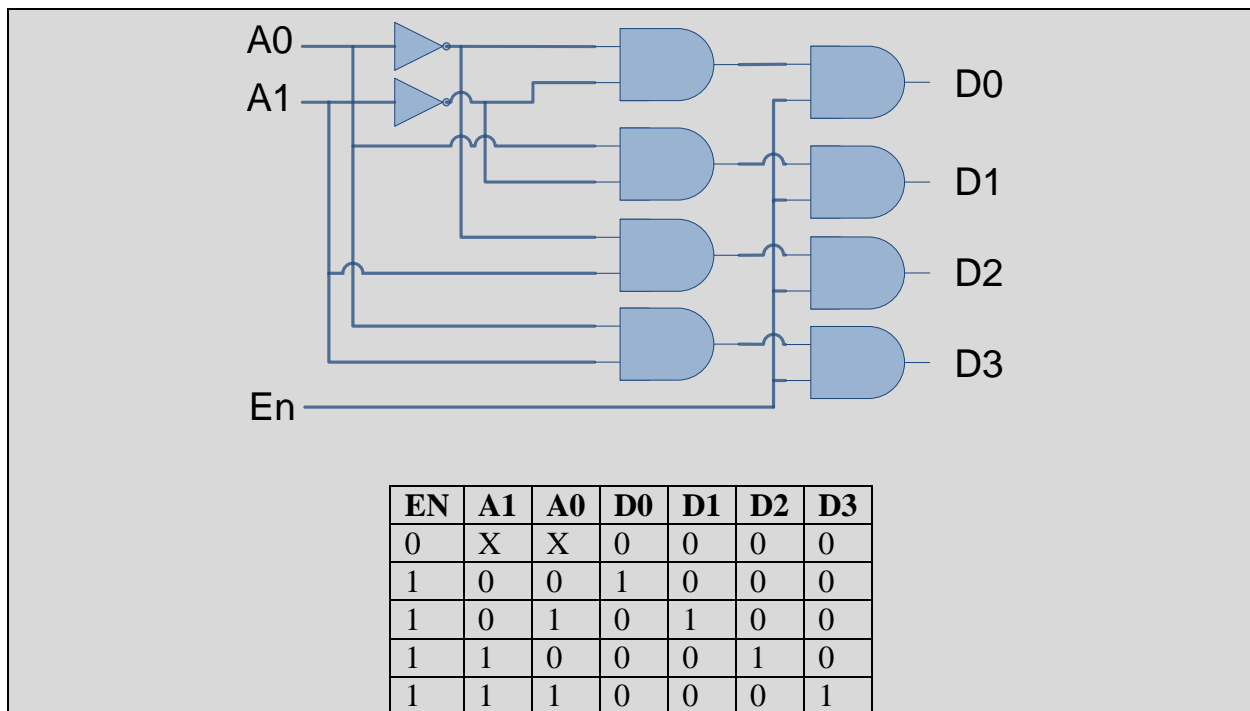Solution**Question 2**

 Assume the initial value of the counters is “1000”. How many different states each counter performs?






Solution

- a) 1000 \rightarrow 0100 \rightarrow 0010 \rightarrow 1001 \rightarrow 1100 \rightarrow 0110 \rightarrow 1011 \rightarrow 0101 \rightarrow 1010 \rightarrow 1101 \rightarrow 1110 \rightarrow 1111 \rightarrow 0111 \rightarrow 0011 \rightarrow 0001 \rightarrow **1000** (15 states).
 b) 1000 \rightarrow 0100 \rightarrow 0010 \rightarrow 0001 \rightarrow 1000 (4 states).

  Question 3




The D flip-flop shown in figure below is a positive edge-triggered flip-flop. For given waveforms at the input, sketch D, Q and X.



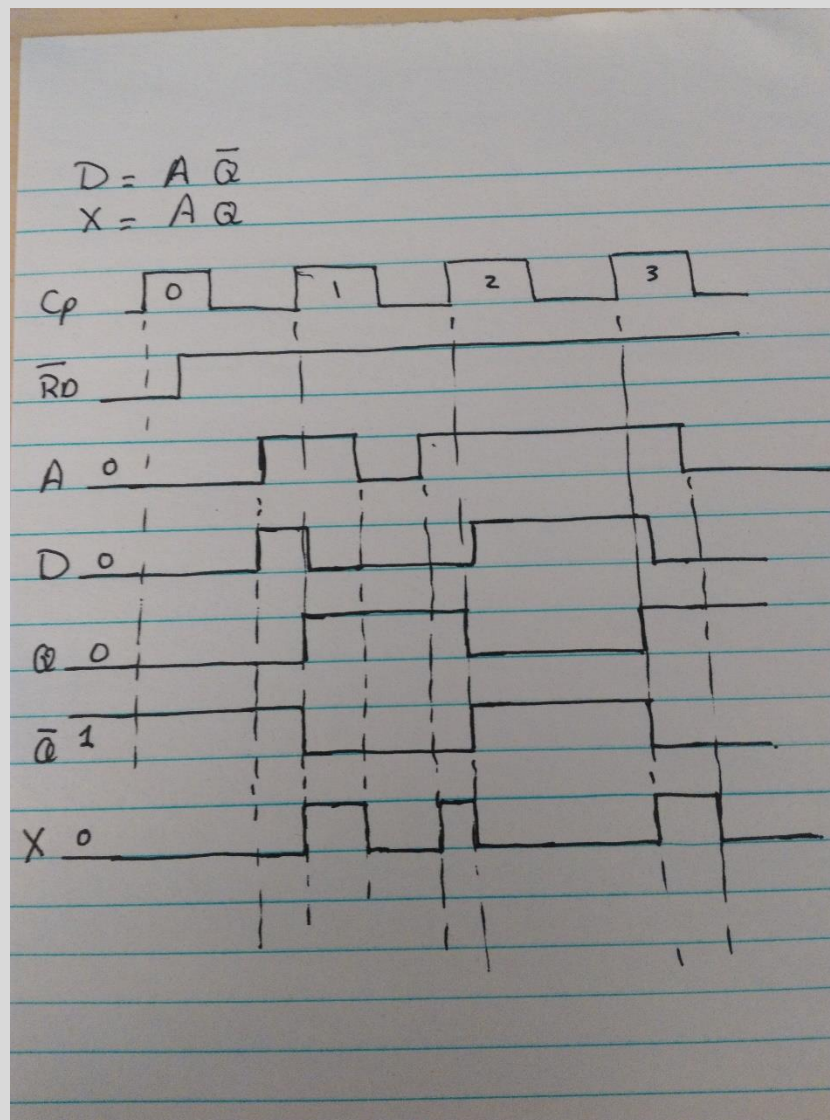Solution

Question 4

Draw timing diagrams for the counter below:

 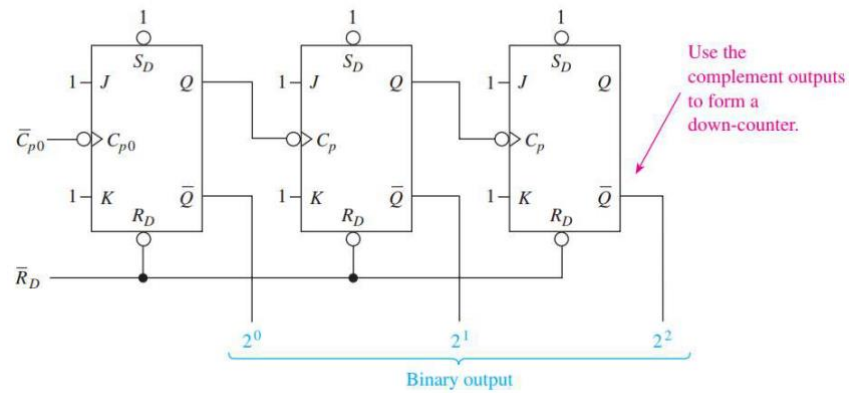 **Solution**

Question 5 (Chu 4.6)

We wish to design a shift-left circuit manually. The inputs include a, which is an 8-bit signal to be shifted, and ctrl, which is a 3-bit signal specifying the amount to be shifted. Both are with the std_logic_vector data type. The output y is an 8-bit signal with the std_logic_vector data type. Use concurrent signal assignment statements to derive the circuit and draw the conceptual diagram.

Solution

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift_left is
5  port(
6      a: in std_logic_vector(7 downto 0);
7      ctrl: in std_logic_vector(2 downto 0);
8      y: out std_logic_vector(7 downto 0)
9  );
10 end shift_left ;
11
12 architecture beh_arch of shift_left is
13 begin
14     with ctrl select
15         y <= a                                when "000",
16             a(6 downto 0) & "0"                when "001",
17             a(5 downto 0) & "00"               when "010",
18             a(4 downto 0) & "000"              when "011",
19             a(3 downto 0) & "0000"             when "100",
20             a(2 downto 0) & "00000"           when "101",
21             a(1 downto 0) & "000000"          when "110",
22             a(0) & "0000000"                 when others; -- 111
23 end beh_arch ;

```