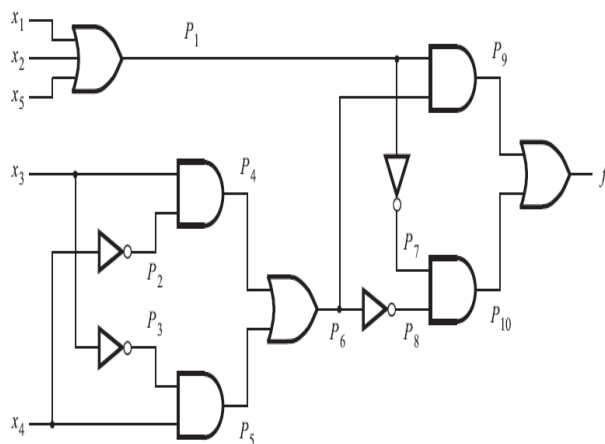


## CEG3155: DGD 6

## Solution of Quiz

**Question1:** For the circuit shown in Figure 1, write the expression of the output signal  $f$ .



$$\begin{aligned}
 P_1 &= x_1 + x_2 + x_5 \\
 P_2 &= \bar{x}_4 & P_4 &= x_3 P_2 \\
 P_3 &= \bar{x}_3 & &= x_3 \bar{x}_4 \\
 P_5 &= P_3 x_4 = \bar{x}_3 x_4 \\
 P_6 &= P_4 + P_5 \\
 &= x_3 \bar{x}_4 + \bar{x}_3 x_4 \\
 P_7 &= \bar{P}_1 = \overline{(x_1 + x_2 + x_5)} \\
 &= \bar{x}_1 \bar{x}_2 \bar{x}_5 \\
 P_8 &= \bar{P}_6 = \overline{(x_3 \bar{x}_4 + \bar{x}_3 x_4)} \\
 P_9 &= P_1 P_6 = (x_1 + x_2 + x_5)(x_3 \bar{x}_4 + \bar{x}_3 x_4) \\
 P_{10} &= P_7 P_8 \\
 &= (\bar{x}_1 \bar{x}_2 \bar{x}_5)(x_3 \bar{x}_4 + \bar{x}_3 x_4) \\
 f &= P_9 + P_{10}
 \end{aligned}$$

**Question 2:**

- a) Convert this structural VHDL code into schematic (similar problem and its block diagram are shown in Figure 2 on page 3 for even-parity detector).

```


1  -- 2-to-4 Line Decoder; structural VHDL Description
2  library ieee;
3  use ieee.std_logic_1164.all
4
5  entity decoder_2_4_w_enable is
6  port(
7      EN, A0, A1 : in std_logic;
8      D0, D1, D2, D3 : out std_logic
9  );
10 end decoder_2_to_4_w_enable;
11
12 architecture structural1_1 of decoder_2_to_4_w_enable is
13     component NOT1
14     port(
15         in1: in std_logic;
16         out1: out std_logic
17     );
18     end component;
19
20     component AND2
21     port(
22         in1, in2: in std_logic;
23         out1: out std_logic
24     );
25     end component;
26
27     signal A0_n, A1_n, N0, N1, N2, N3: std_logic;
28     begin
29         g0: NOT1 port map (in1 => A0, out1 => A0_n);
30         g1: NOT1 port map (in1 => A1, out1 => A1_n);
31         g2: AND2 port map (in1 => A0_n, in2 => A1_n, out1 => N0);
32         g3: AND2 port map (in1 => A0, in2 => A1_n, out1 => N1);
33         g4: AND2 port map (in1 => A0_n, in2 => A1, out1 => N2);
34         g5: AND2 port map (in1 => A0, in2 => A1, out1 => N3);
35         g6: AND2 port map (in1 => EN, in2 => N0, out1 => D0);
36         g7: AND2 port map (in1 => EN, in2 => N1, out1 => D1);
37         g8: AND2 port map (in1 => EN, in2 => N2, out1 => D2);
38         g9: AND2 port map (in1 => EN, in2 => N3, out1 => D3);
39     end structural_1;
40

```

b) Fill the truth table for the schematic from part a)
 
### Solution

The conceptual diagram can be using logic gates or blocks that indicate the type of gate. Both solutions are correct.



EN	A1	A0	D0	D1	D2	D3
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

**Chapter 6****Question 1 (Chu 6.3)**

One way to specify a combinational circuit is to describe its function by a truth table, in which we list all possible input combinations and their desired output values. Assume that the circuit has  $n$  inputs.

- What is the size (number of the rows) of the table?
- What is the problem with this approach?

**Solution**

- $2^n$
- The number of rows grows exponentially.

**Question 2 (Chu 6.4)**

Assume that  $a$  and  $b$  are 3-bit inputs (let  $a$  be  $a_2a_1a_0$  and  $b$  be  $b_2b_1b_0$ ).

- Determine the Boolean expression for the relational operation  $a > b$ .
- Assume that  $b$  is a constant and that  $b = "101"$ . Determine the Boolean expression again.
- Assume that  $a$  is a constant and that  $a = "101"$ . Determine the Boolean expression again.

**Solution**

- $a_2b'_2 + (a_2 \oplus b_2)' a_1b'_1 + (a_2 \oplus b_2)'(a_1 \oplus b_1)' a_0b'_0$
- $a_2 a_1$
- $b'_2 + b'_0 b_2 b'_1$