

## CEG3155: DGD 7

## Chapter 7

**Question 1 (Chu 7.1)**

Consider an arithmetic circuit that can perform four operations:  $(a+b)$ ,  $(a-b)$ ,  $(a+1)$  and  $(a-1)$ , where  $a$  and  $b$  are 16-bit unsigned numbers and the desired operation is specified by a 2-bit control signal,  $ctrl$ .

- Design the circuit using two adders, one incrementor and one decrementor. Derive the VHDL code.
- Design the circuit using only one adder. Derive the VHDL code.

**Solution**

a)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity prob71 is
6  port (
7      a,b: in std_logic_vector(15 downto 0);
8      ctrl: in std_logic_vector(1 downto 0);
9      y: out std_logic_vector(15 downto 0)
10 );
11 end prob71;
12
13 architecture direct_arch of prob71 is
14     signal au, bu, yu: unsigned(15 downto 0);
15 begin
16     au <= unsigned(a);
17     bu <= unsigned(b);
18     with ctrl select
19         yu <= au+bu when "00",
20             au-bu when "01",
21             au+1 when "10",
22             au-1 when others;
23     y <= std_logic_vector(yu);
24 end direct_arch;
25

```

b)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity prob71 is
6  port (
7      a,b: in std_logic_vector(15 downto 0);
8      ctrl: in std_logic_vector(1 downto 0);
9      y: out std_logic_vector(15 downto 0)
10 );
11 end prob71;
12
13 architecture effi_arch of prob71 is
14     signal src0, src1: unsigned(15 downto 0);
15     signal cin: unsigned(0 downto 0);
16 begin
17     src0 <= unsigned(a);
18     with ctrl select
19         src1 <= unsigned(b) when "00",
20             unsigned(not b) when "01",
21             "0000000000000001" when "10",
22             "1111111111111111" when others;
23     cin <= "1" when ctrl="01" else "0";
24     y <= std_logic_vector(src0 + src1 + cin);
25 end effi_arch;

```

**Question 2 (Chu 7.2)**

Design a circuit that converts an 8-bit signed input to 8-bit sign-magnitude output (where the MSB is the sign bit and the remaining 7 bits are magnitude). Use a minimal number of relational and arithmetic operators in your design. Draw the top-level diagram and derive the VHDL code.

*Solution*

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity prob72 is
6  port (
7      a: in std_logic_vector(7 downto 0);
8      y: out std_logic_vector(7 downto 0)
9  );
10 end prob72;
11
12 architecture arch of prob72 is
13     signal a_neg: std_logic_vector(7 downto 0);
14 begin
15     -- no change if a is positive]
16     -- negative a to obtain magnitude if a is negative
17     a_neg <= std_logic_vector(0 - signed(a));
18     y <= (a(7) & a_neg(6 downto 0)) when a(7)='1' else
19         a;
20 end arch;
21

```

**Question 3 (Chu 7.4)**

Consider a 16-bit shifting circuit that can perform rotating right or rotating left. Use selected signal assignment statements to implement the shifting function.

- Design the circuit using one rotate-right circuit, one rotate-left circuit and one 2-to-1 multiplexer to select the desired result. Derive the VHDL code.
- Design the circuit using one rotate-right circuit with a pre- and post-processing reversing circuit. The reversing circuit either passes the original input or reverses the input bit-wise (e.g., if a 4-bit input  $a_3a_2a_1a_0$  is used, the reversed output becomes  $(a_0a_1a_2a_3)$ ). Derive the VHDL code.

*Solution*

a)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity prob74 is
6  port (
7      a: in std_logic_vector(15 downto 0);
8      RR: in std_logic;
9      y: out std_logic_vector(15 downto 0)
10 );
11 end prob74;
12
13 architecture arch of prob74 is
14     aR, aL: std_logic_vector(15 downto 0);
15
16     component rotateRight is
17     port(
18         a: in std_logic_vector(15 downto 0);
19         y: out std_logic_vector(15 downto 0)
20     );
21     end component;
22
23     component rotateLeft is
24     port(
25         a: in std_logic_vector(15 downto 0);
26         y: out std_logic_vector(15 downto 0)
27     );
28     end component;
29
30     component mux2to1 is
31     port(
32         a, b: in std_logic_vector(15 downto 0);
33         s: in std_logic;
34         y: out std_logic_vector(15 downto 0)
35     );
36     end component;
37 begin
38     L1: rotateRight port map(a, aR);
39     L2: rotateLeft port map(a, aL);
40     L3: mux2to1 port map(aR, aL, RR, y);
41 end arch;
42

```

b)

```


1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity prob74 is
6  port (
7      a: in std_logic_vector(15 downto 0);
8      RR: in std_logic;
9      y: out std_logic_vector(15 downto 0)
10 );
11 end prob74;
12
13 architecture arch of prob74 is
14     aR, aRR: std_logic_vector(15 downto 0);
15
16     component rotateRight is
17     port(
18         a: in std_logic_vector(15 downto 0);
19         y: out std_logic_vector(15 downto 0)
20     );
21     end component;
22
23     component reverse is
24     port(
25         a: in std_logic_vector(15 downto 0);
26         r: in std_logic;           -- reverse if r = 1
27         y: out std_logic_vector(15 downto 0)
28     );
29     end component;
30 begin
31     L1: reverse port map(a, RR, aR);
32     L2: rotateRight port map(aR, aRR);
33     L3: reverse port map(aRR, RR, y);
34 end arch;
35

```


**Question 4 (Chu 7.8)**

Design a 16-bit rotate-left shifting circuit using the multilevel structure discussed in Section 7.4.4.

Example (Section 7.4.4):

 


**Figure 7.11** Barrel shifter using a single level of 8-to-1 multiplexers.

  

(b) Detailed diagram

**Figure 7.12** Barrel shifter using three levels of 2-to-1 multiplexers.



(a) Block diagram

*Solution*

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity prob78 is
5  port(
6      a: in std_logic_vector(15 downto 0);
7      amt: in std_logic_vector(3 downto 0);
8      y: out std_logic_vector(15 downto 0)
9  );
10 end prob78;
11
12 architecture multi_level_arch of prob78 is
13     signal le0_out, le1_out, le2_out, le3_out: std_logic_vector(15 downto 0);
14 begin
15     -- level 0, shift 0 or 1 bit
16     le0_out <= a(14 downto 0) & a(15) when amt(0)='1' else
17         a;
18     -- level 1, shift 0 or 2 bits
19     le1_out <=
20         le0_out(13 downto 0) & le0_out(15 downto 14) when amt(1)='1' else
21         le0_out;
22     -- level 2, shift 0 or 4 bits
23     le2_out <=
24         le1_out(11 downto 0) & le1_out(15 downto 12) when amt(2)='1' else
25         le1_out;
26     -- level 3, shift 0 or 8 bits
27     le3_out <=
28         le2_out(7 downto 0) & le2_out(15 downto 8) when amt(3)='1' else
29         le2_out;
30     y <= le3_out;
31 end multi_level_arch;
32
```