

## CEG3155: DGD 4

## Questions


**Question 1 (Chu 5.5)**

Derive the conceptual diagram for the following code segment:

```

3  if (a > b and op="00") then
4      y <= a - b;
5      z <= a - 1;
6      status <= '0';
7  else
8      y <= b - a;
9      z <= b - 1;
10     status <= '1';
11 end if;
12

```

 *Solution***Question 2 (Chu 5.8)**

Consider the following code segment:

```

3  if (a > b) then
4      y <= a - b;
5  else
6      if(a > c)
7          y <= a - c;
8      else
9          y <= a + 1;
10     end if;
11 end if;
12

```

- Draw the conceptual diagram.
- Rewrite the code using two concurrent conditional signal assignment statements.
- Rewrite the code using one concurrent conditional signal assignment statement.
- Rewrite the code using one case statement.

*Solution*

a)

b)

```

y_tmp <= a - c when a > c else
    a + 1;
y <= a - b when a > b else
    y_tmp;
  
```

c)

```

y <= a - b when a > b else
    a - c when a > c else
    a + 1;
  
```

d)

```

tmp(1) <= '1' when a > b else '0';
tmp(0) <= '1' when a > c else '0';
...
case tmp is
    when "11"|"10" => y <= a - b;
    when "01"      => y <= a - c;
    when others    => y <= a - 1;
end case;
  
```

**Question 3 (Chu 5.12)**

Consider the shift-left circuit discussed in Problem 4.6. The inputs include a, which is an 8-bit signal to be shifted, and ctrl, which is a 3-bit signal specifying the amount to be shifted. Both are with the std\_logic\_vector data type. The output y is an 8-bit signal with the std\_logic\_vector data type. Use a case statement to derive the circuit and draw the conceptual diagram.

**Solution**

```

-- 8-bit shift left circuit

library ieee;
use ieee.std_logic_1164.all;

entity shift_left is
    port(
        a: in std_logic_vector(7 downto 0);
        ctrl: in std_logic_vector(2 downto 0);
        y: out std_logic_vector(7 downto 0)
    );
end shift_left ;

architecture case_arch of shift_left is
begin
    process(ctrl,a)
    begin
        case ctrl is
            when "000" => y <= a;
            when "001" =>
                y <= a(6 downto 0) & "0";
            when "010" =>
                y <= a(5 downto 0) & "00";
            when "011" => "="
                y <= a(4 downto 0) & "000";
            when "100"=> "="
                y <= a(3 downto 0) & "0000";
            when "101" => "="
                y <= a(2 downto 0) & "00000";
            when "110" => "="
                y <= a(1 downto 0) & "000000";
            when others => "="
                y <= a(0) & "0000000";
        end case;
    end process;
end case_arch ;

```

**Question 4**

Using a conditional signal assignment, write VHDL code for an 8-to-3 priority encoder.

**Solution**

Priority encoder works as follows: If two or more single-bit inputs are at logic 1, the input with the high priority will have effect.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity priEnc is
6  port (
7      A: In unsigned (7 downto 0);
8      Y: out unsigned (2 downto 0)
9      Valid: out std_logic;
10 );
11 end priEnc;
12
13 architecture priEnc_arch of priEnc is
14 begin
15     Y <= "000" when A(0) = '1' else
16         "001" when A(1) = '1' else
17         "010" when A(2) = '1' else
18         "011" when A(3) = '1' else
19         "100" when A(4) = '1' else
20         "101" when A(5) = '1' else
21         "110" when A(6) = '1' else
22         "111" when A(7) = '1' else
23         "XXX";
24 end priEnc_arch;
25

```

**Question 5**

Explain the difference between these two VHDL statements and show their conceptual implementations (i.e. draw the circuits):

```



3  if (a='1') then
4      dout <= c;
5  elsif (b='1')
6      dout <= d;
7  else
8      dout <= e;
9  end if;

```

```

3  ab <= a & b;
4  case ab is
5      when "10"|"11" => dout <= c;
6      when "01" => dout <= d;
7      when others => dout <= e;
8  end case;
9

```

  **Solution***For the code on the left:**For the code on the right:***Question 6**

Rewrite the combinational VHDL code given below so that it uses one adder. Show the conceptual diagram (i.e. draw the circuit) of both designs.

```

with sel_exp select
  r <= a+b when "00",
      a+c when "01",
      d+1  when others;

```

**Solution**


```

with sel_exp select
  temp1 <= a when "00"|"01",
           d when others;
  temp2 <= b when "00",
           c when "01",
           1 when others;

```

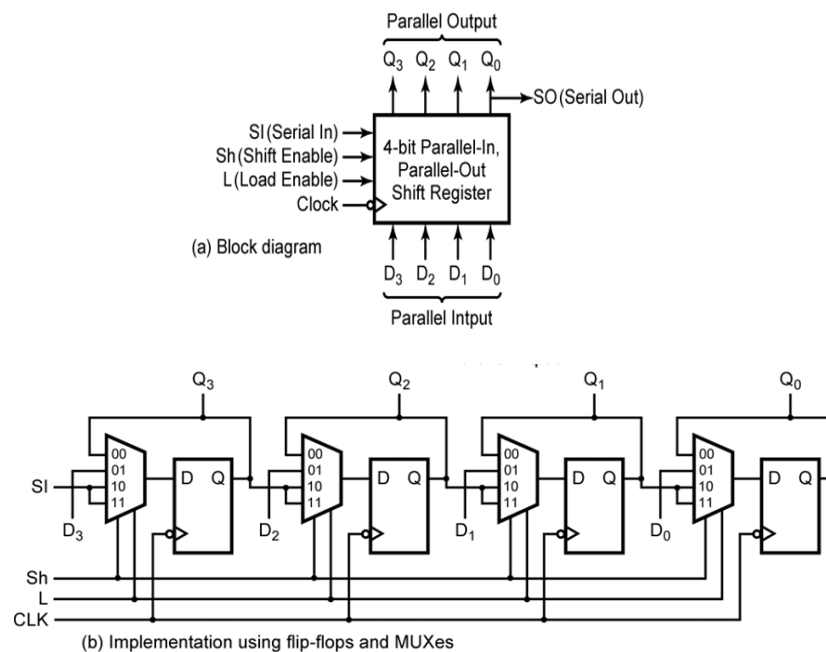**Question 7**

The following figure shows a parallel-in parallel out right shift register, Part a is the block diagram and part b is the implementation using flip flops and multiplexers



Inputs		Next State				Action
Sh (Shift)	Ld (Load)	Q <sub>3</sub> <sup>+</sup>	Q <sub>2</sub> <sup>+</sup>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>	
0	0	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	no change
0	1	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	load
1	X	SI	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	right shift


Show how to make the shift register reverse the order of its bits: i.e.  $Q_3^+ = Q_0$ ,  $Q_2^+ = Q_1$ ,  $Q_1^+ = Q_2$ ,  $Q_0^+ = Q_3$

- Use external connections between the Q output and D inputs, what should the values of sh and L be for a reversal?
- Change the internal circuitry to allow bit reversal, so that the D inputs may be used for other purposes. Replace Sh and L with A and B and the register operate according to the following table:

Inputs A B	Next states Q <sub>3</sub> <sup>+</sup> Q <sub>2</sub> <sup>+</sup> Q <sub>1</sub> <sup>+</sup> Q <sub>0</sub> <sup>+</sup>	Action
0 0	Q <sub>3</sub> Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub>	No
0 1	D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub>	Load
1 0	SI Q <sub>3</sub> Q <sub>2</sub> Q <sub>1</sub>	Right shift
1 1	Q <sub>0</sub> Q <sub>1</sub> Q <sub>2</sub> Q <sub>3</sub>	Reverse bits

*Solution*

1.

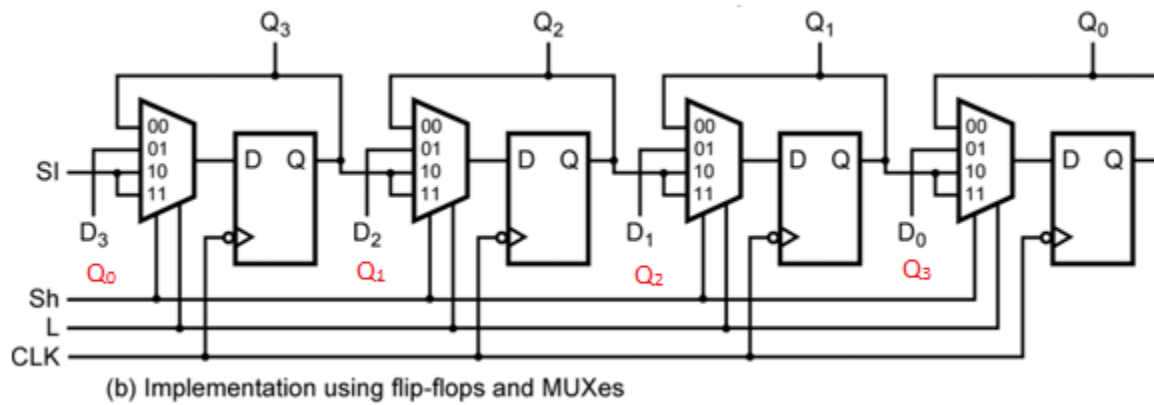

2.

